

EN1012 Electronic Devices and Circuits Topic 5 - Amplifier Circuits and Applications

Upeka Premaratne

Department of Electronic and Telecommunication Engineering

October 16, 2017


Introduction

Outline

- 1 Introduction
- 2 Voltage Amplifiers
- 3 Current Amplifiers
- 4 Conclusion


Amplification

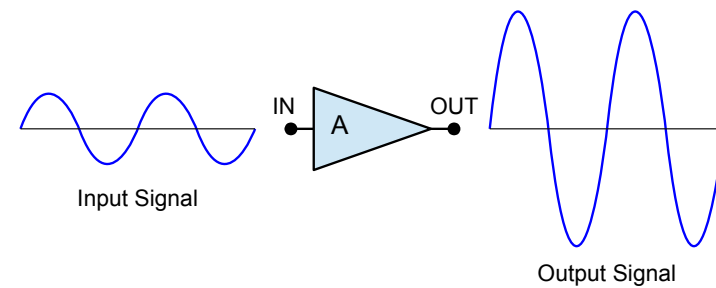- Increasing the amplitude of a signal
 - Increasing the voltage, current or power of a signal



Attenuation

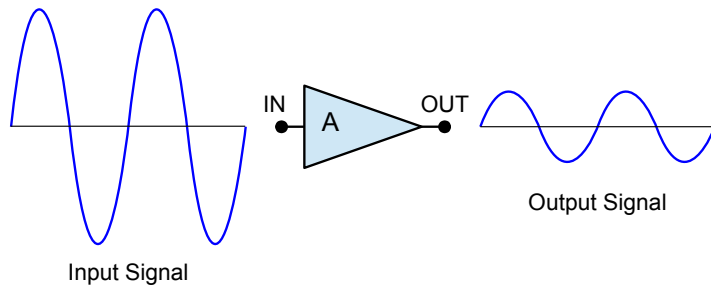- Decreasing the amplitude of a signal
 - ▶ Filtering of signals (e.g. removing 50 Hz AC line noise)



Amplifier Parameters

- Input impedance
 - ▶ Made as large as possible to prevent current loading and maximize voltage transfer
- Output impedance
 - ▶ Often made as small as possible to maximize power output
- Gain of the amplifier
 - ▶ Limited by the saturation of the device
 - ▶ Optimal at the bandwidth of the amplifier
 - ▶ Typical ranges: 20-20000 Hz for an audio amplifier, 0.1-100 Hz for a seismic signal amplifier

Nature of the Amplifier


- Voltage (Pre) amplifiers
 - ▶ Provide voltage gain
 - ▶ Suitable for amplifying weak signals
- Current (Power) amplifiers
 - ▶ Provide current gain to a large amplitude voltage signals, resulting in power gain
 - ▶ Suitable for driving loads such as speakers and radio transmitters

Voltage Amplifiers

Operational Amplifiers

- The main device for voltage amplification
- A *monolithic* amplifier implemented on a single chip
 - The basic building blocks are transistor amplifiers
- Unlike discrete BJT or FET amplifiers it is convenient to use
 - The gain of an op-amp amplifier can be conveniently set
- It has a number of other applications
 - Comparators
 - Hysteresis comparators
 - High impedance buffers etc.
- Generally needs a *dual supply* for amplification
- Suitable for low frequency use


Op-Amp Model

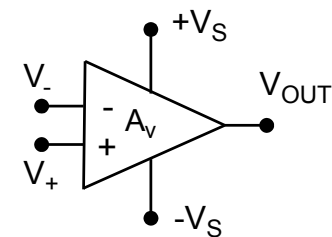


- Two inputs V_+ (non-inverting input) and V_- (inverting input)
- Has a very high voltage gain A_V (typically 10^5 to 10^6)
- The difference $\Delta V = V_+ - V_- \approx 0$ (considered to be very small)

Op-Amp Model (Contd..)

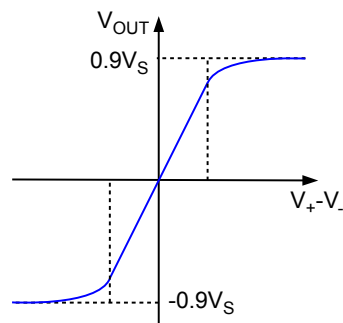- Very high input impedance
 - Negligible current flows into the device
- Very low output impedance
- The output is given by
 - $V_{OUT} = A_V(V_+ - V_-)$
 - It saturates when $V_{OUT} \approx 0.9V_S$



Inverting Amplifier

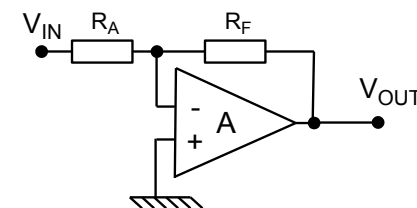


$$V_+ - V_- \approx 0 \Rightarrow V_- \approx 0 \text{ A virtual ground}$$

Therefore,


$$G \approx \frac{V_{OUT}}{V_{IN}} = \frac{-I_F R_F}{I_F R_A} = -\frac{R_F}{R_A}$$

Inverting Amplifier Output

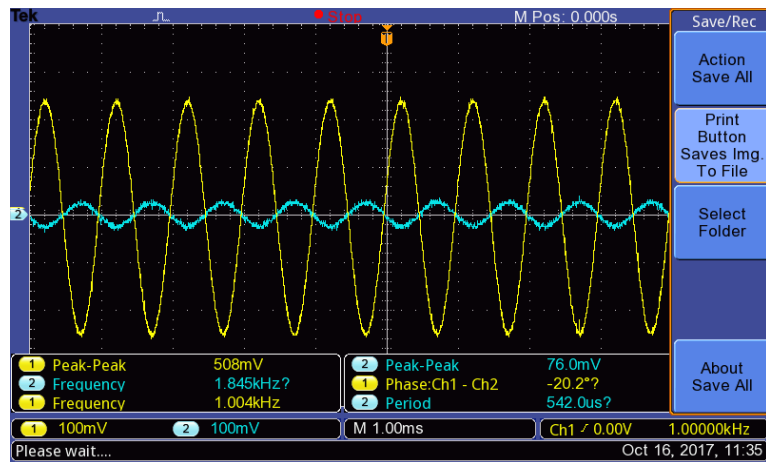


Navigation icons: back, forward, search, etc.

Non-Inverting Amplifier Output

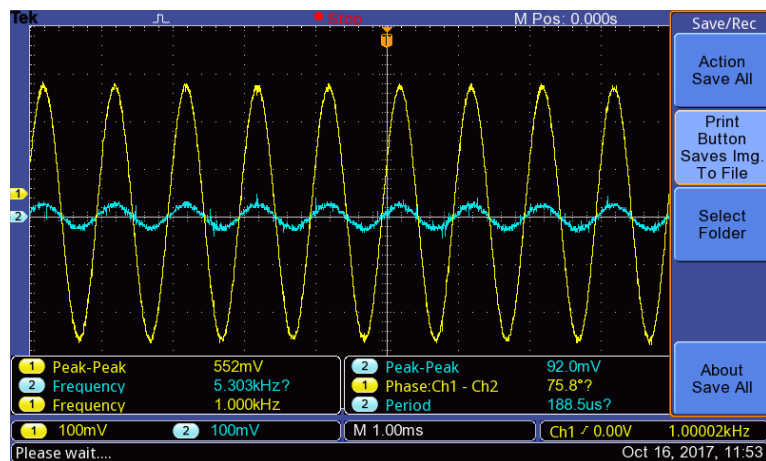

Navigation icons: back, forward, search, etc.

Non-Inverting Amplifier

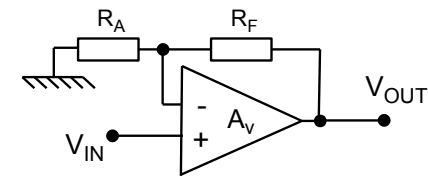


$$V_{OUT} = A_V [V_+ - V_-] = A_V \left[V_+ - \frac{R_A}{(R_A + R_F)} V_{OUT} \right]$$

$$\frac{V_{OUT}}{A_V} = \left[V_{IN} - \frac{R_A}{(R_A + R_F)} V_{OUT} \right] \approx 0 \Rightarrow G = \frac{R_F}{R_A} + 1$$

Navigation icons: back, forward, search, etc.

High Impedance Buffer

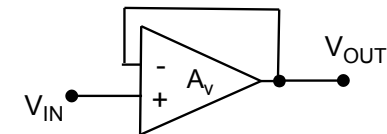

$$V_{OUT} = A_V [V_+ - V_-] = A_V [V_{IN} - V_{OUT}]$$

$$\frac{V_{OUT}}{A_V} = [V_{IN} - V_{OUT}] \approx 0 \Rightarrow G = 1$$


- Can match a high impedance source to a low impedance load

Navigation icons: back, forward, search, etc.


Comparator

- In the comparator the op-amp is used in open-loop
 - ▶ Maximum gain
 - ▶ Will saturate for a low difference
 - ▶ For example: $A_V = 10^5$ and $V_S = \pm 12\text{ V}$ and $V_{SAT} = 0.9V_S$ results in maximum signal amplitude (δ) of $108\text{ }\mu\text{V}$
- Therefore, by comparing V_+ and V_- it is possible to compare the two and switch a device on and off.
 - ▶ If $V_+ - V_- > \delta$ then $V_{OUT} = +V_{SAT}$
 - ▶ If $V_- - V_+ > \delta$ then $V_{OUT} = -V_{SAT}$


LDR Comparator Circuit

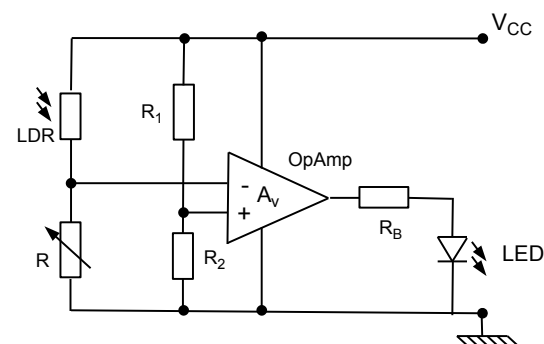

Thermistor Comparator Circuit

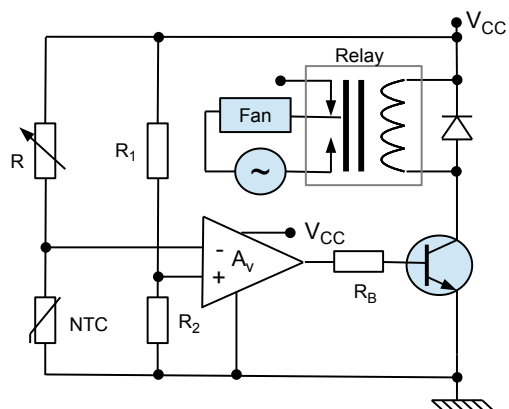

Hysteresis Comparator

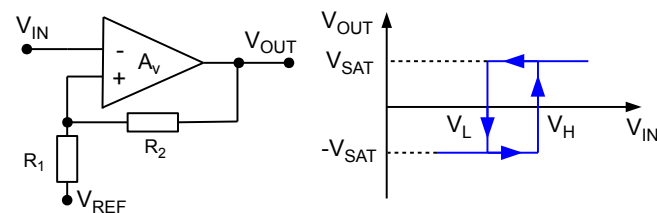

$$V_H = \frac{R_2 V_{REF} + R_1 V_{SAT}}{R_1 + R_2}$$

$$V_L = \frac{R_2 V_{REF} - R_1 V_{SAT}}{R_1 + R_2}$$

Hysteresis Comparator (Contd..)

Obtained using the *Superposition theorem* because (+)-input is considered as $I_{IN} \neq 0$ due to saturation.

$$\text{When } V_{REF} = 0, V_+ = V_1 = \frac{R_1}{R_1 + R_2} V_{OUT} = \pm \frac{R_1}{R_1 + R_2} V_S$$

$$\text{When } V_{OUT} = 0, V_+ = V_2 = \frac{R_1}{R_1 + R_2} V_{REF}$$

From the Superposition Theorem (since R_1 and R_2 are linear)

$$V_+ = V_1 + V_2 = \underbrace{\pm \frac{R_1}{R_1 + R_2} V_S}_{\text{positive feedback}} + \underbrace{\frac{R_2}{R_1 + R_2} V_{REF}}_{\text{offset}}$$


Therefore V_+ can either be V_H or V_L .

Transistor Power Amplifiers


- Generally op-amps are not capable of driving large loads
 - ▶ Have to use transistor amplifiers instead
- Signal amplitude is large enough to affect the bias point of the transistors used
- Example circuit is the Class AB power amplifier
 - ▶ Has two complementary BJTs (one for each half cycle)

Current Amplifiers



Class AB Power Amplifier

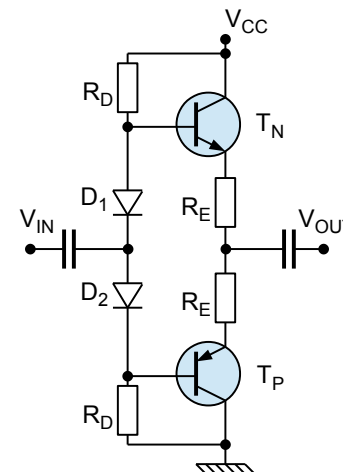

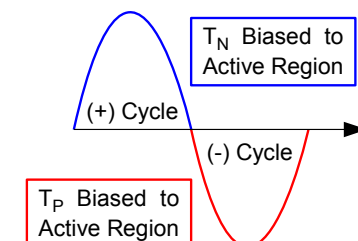- R_E prevents thermal runaway
- Diode AC resistance is considered negligible
- $R_D \approx 1k\Omega$





Further Current Amplification

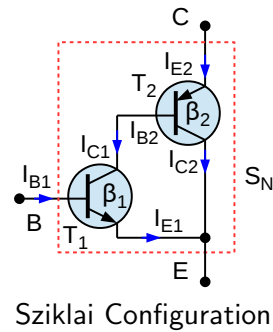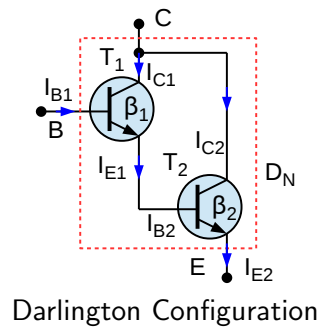

Conclusion

Further Current Amplification (Contd..)

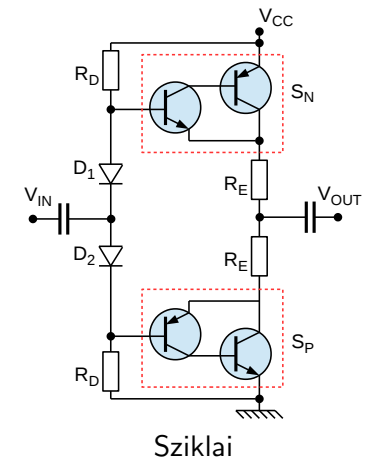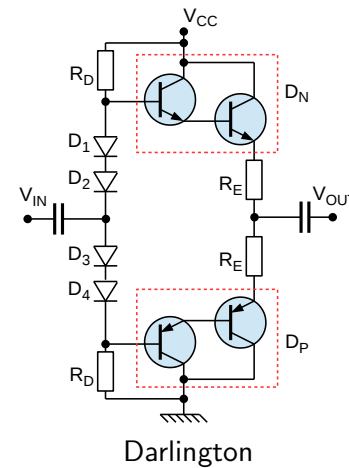

Summary

- Transistors can be used for switching and amplification
- Switching circuits are simple to design
- Amplifier circuits are more complex
 - ▶ Simple amplifier bias circuits have many drawbacks
 - ▶ Robust amplifier bias circuits are difficult to design
- Op-amps are general purpose amplifiers that are convenient to implement
 - ▶ Even these devices have circuits that are complex to design
- What are the limitations of analog electronics?
 - ▶ For example, can a *Turing Machine* be built using analog components?

Next Lecture...

Introduction to Digital Electronics